 


Decoder and Encoder

Theory


- Combinational Circuit
- *Decodes* the given input
- Input: n bits
- Output: 2^n bits

General Block Diagram – n to m decoder




Each output corresponds to **one** of the 2^n possible combinations, $m=2^n$

General Block Diagram

 

- The ENABLE line performs no logical operation
- Used to toggle decoder between ACTIVE and INACTIVE states
 - When enable input is 0, all outputs are 0

2-to-4 line decoder

 

- 2 inputs A_1 (MSB) and A_0 (LSB),

- $2^2=4$ outputs

D_0 , D_1 , D_2 and D_3

Truth Table – without ENABLE

Decimal #	Input		Output			
	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	0	1	0	0	0
1	0	1	0	1	0	0
2	1	0	0	0	1	0
3	1	1	0	0	0	1

- For each input combination, one single output line is activated(=1)
- Each output is actually a MINTERM by taking a certain combination of the inputs


- $D_0 = A_1' A_0'$, (minterm m 0) which corresponds to input 00
- $D_1 = A_1' A_0$, (minterm m 1) which corresponds to input 01
- $D_2 = A_1 A_0'$, (minterm m 2) which corresponds to input 10
- $D_3 = A_1 A_0$, (minterm m 3) which corresponds to input 11

Truth Table – with ENABLE


Decimal value	Enable	Inputs		Outputs			
	E	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
	0	X	X	0	0	0	0
0	1	0	0	1	0	0	0
1	1	0	1	0	1	0	0
2	1	1	0	0	0	1	0
3	1	1	1	0	0	0	1

- $D_0 = E A_1' A_0'$, (minterm m 0) which corresponds to input 00
- $D_1 = E A_1' A_0$, (minterm m 1) which corresponds to input 01
- $D_2 = E A_1 A_0'$, (minterm m 2) which corresponds to input 10
- $D_3 = E A_1 A_0$, (minterm m 3) which corresponds to input 11

Circuit Diagram – without ENABLE

 


Circuit Diagram – with ENABLE

 

As long as E is 0,
the outputs remain 0


3 to 8 line Decoder

 

Truth Table

Dec. Code	Inputs			Outputs							
	A ₂	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0	0	0	0	0
2	0	1	0	0	0	1	0	0	0	0	0
3	0	1	1	0	0	0	1	0	0	0	0
4	1	0	0	0	0	0	0	1	0	0	0
5	1	0	1	0	0	0	0	0	1	0	0
6	1	1	0	0	0	0	0	0	0	1	0
7	1	1	1	0	0	0	0	0	0	0	1

Circuit Diagram

 


Construct a 3-to-8 decoder using two 2-to-4 decoders with enable inputs.

Steps

- The two least significant bits (i.e. A_1 and A_0) are connected to both decoders
- Most significant bit (A_2) is connected to the enable input of one decoder.
- The complement of most significant bit (A_2) is connected to the enable of the other decoder.

Steps

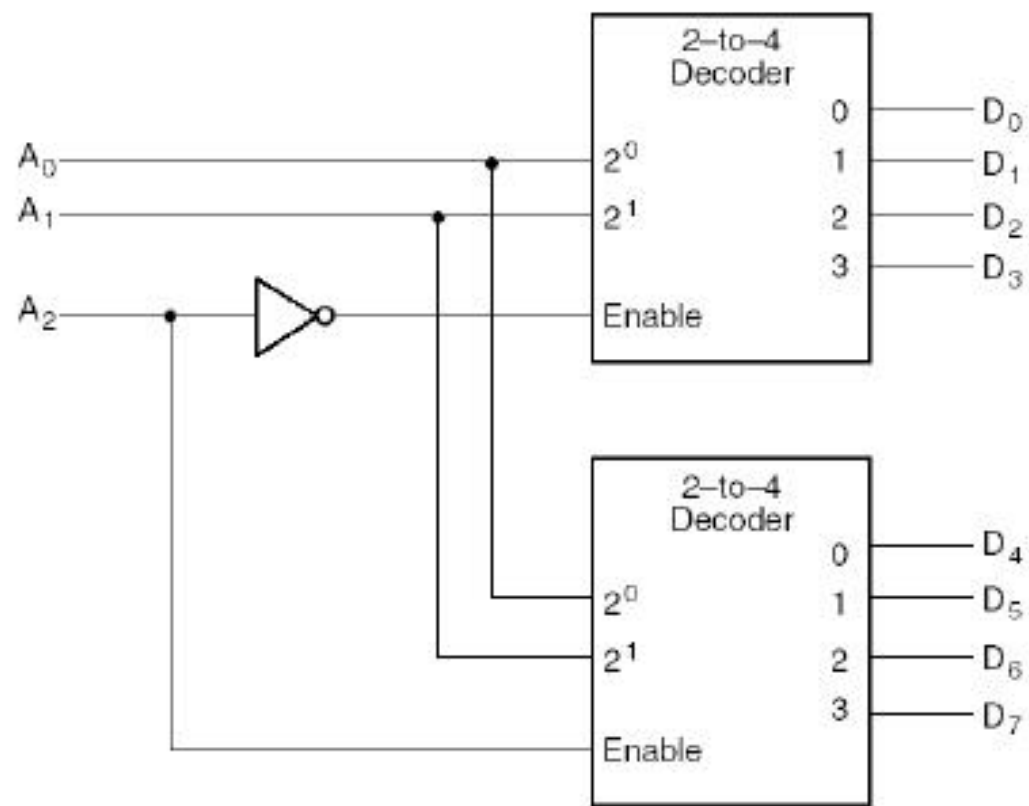
- When $A_2 = 0$, upper decoder is enabled, while the lower is disabled. Thus, the outputs of the upper decoder correspond to minterms D_0 through D_3 .
- When $A_2 = 1$, upper decoder is disabled, while the lower is enabled. Thus, the outputs of the lower decoder correspond to minterms D_4 through D_7 .




Encoder

- Performs reverse operation of Decoder
- 2^n inputs, n outputs
- At any time instant t, only one input can be high (logic 1)
- Output lines generate the binary code corresponding to the high input

General Block Diagram

 


Block Diagram – 8 to 3 Encoder

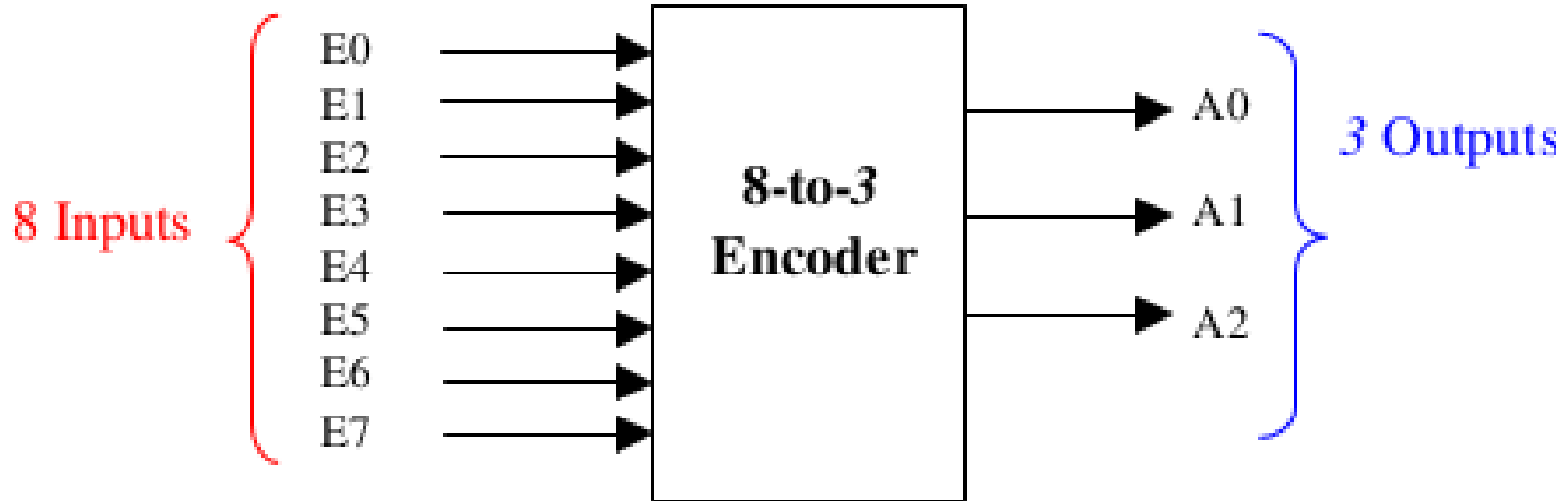

Truth Table

Inputs								Outputs			Decimal Code
E7	E6	E5	E4	E3	E2	E1	E0	A2	A1	A0	
0	0	0	0	0	0	0	0	0	0	0	
0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	1	0	0	0	1	1
0	0	0	0	0	1	0	0	0	1	0	2
0	0	0	0	1	0	0	0	0	1	1	3
0	0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	0	0	0	0	1	0	1	5
0	1	0	0	0	0	0	0	1	1	0	6
1	0	0	0	0	0	0	0	1	1	1	7

4 to 2 Encoder

 

Truth Table

Inputs				Outputs	
D_3	D_2	D_1	D_0	Q_1	Q_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	x	x

Q_0 is high when D_1 or D_3 is high

$$Q_0 = D_1.D_0'.D_2'.D_3' + D_3.D_2'.D_1'.D_0'$$

$$Q_1 = D_2.D_1'.D_3'.D_0' + D_3.D_2'.D_1'.D_0'$$

Circuit Diagram

- Do it yourself !

Problems of Encoders


- If two or more inputs are active at the same time, what should the output be?
- An output of all 0's is generated in 2 cases:
 - when all inputs are 0
 - when E0 is equal to 1.

How can this ambiguity be resolved?

PRIORITY ENCODER

- Uses pre-defined 'priority' value for each input
- If multiple inputs are 1, output will correspond to input pin with highest priority
- Digital Encoders that use this logic, are Priority Encoders
- In the presence of higher priority input, other lower priority inputs are ignored

Block Diagram

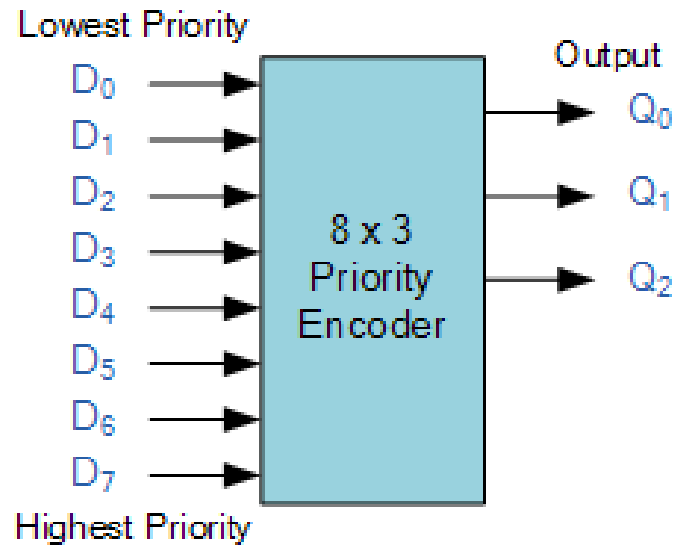

Truth Table

[illegible]

Expressions

Digital Inputs								Binary Output		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	X	0	0	1
0	0	0	0	0	1	X	X	0	1	0
0	0	0	0	1	X	X	X	0	1	1
0	0	0	1	X	X	X	X	1	0	0
0	0	1	X	X	X	X	X	1	0	1
0	1	X	X	X	X	X	X	1	1	0
1	X	X	X	X	X	X	X	1	1	1

$$Q_0 = D_1 + D_3 + D_5 + D_7$$

$$Q_1 = D_2 + D_3 + D_6 + D_7$$

$$Q_2 = D_4 + D_5 + D_6 + D_7$$

Priority Encoder

